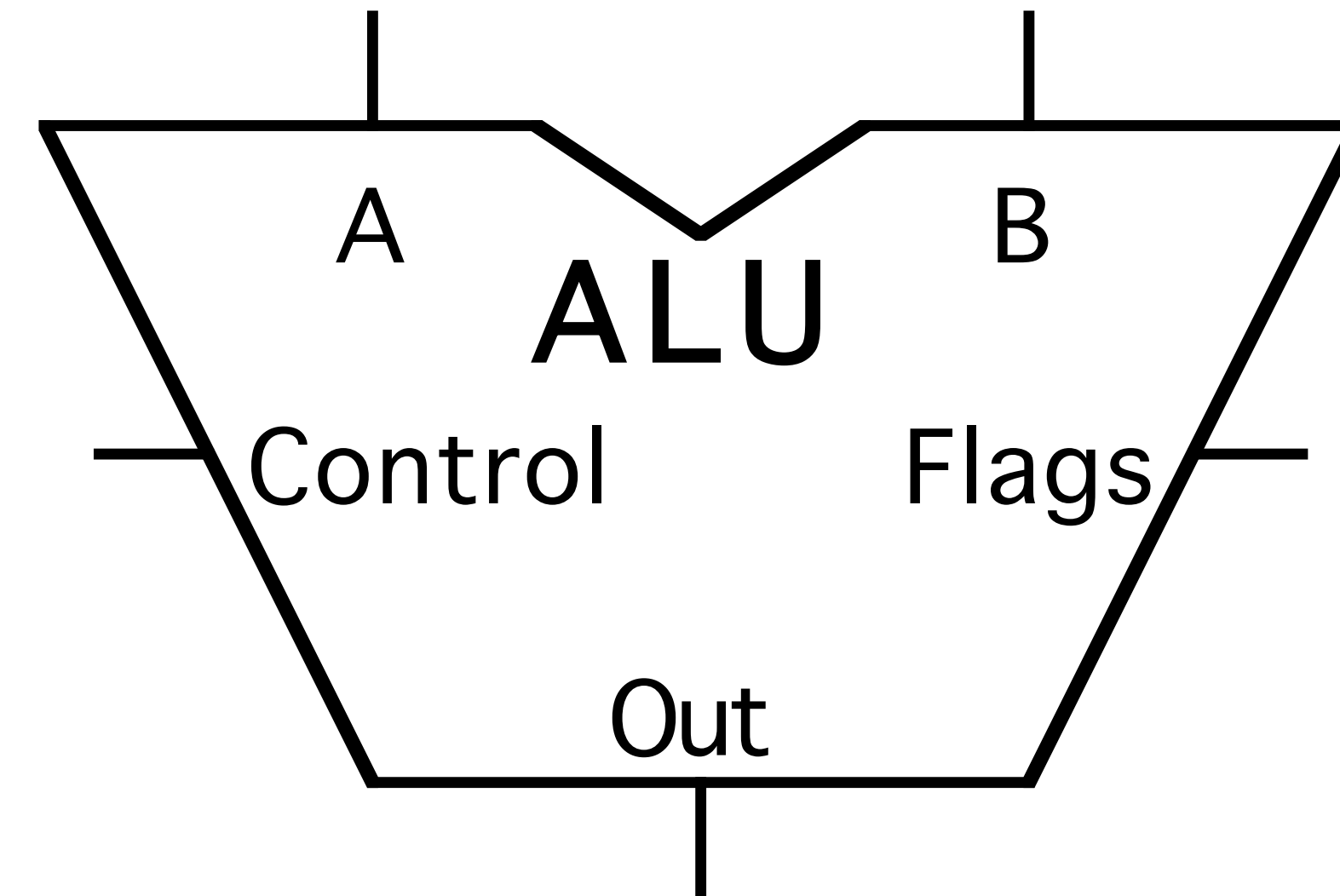


# Arithmetic and Logic

Mano chapter 3

# ALU

- Arithmetic Logic Unit
  - Arithmetic: ADD, SUB, MULT, DIV
  - Logic: AND, OR, NOT, XOR
- Mathematical "heart" of the computer
- We know how to built a circuit that can add, and do logic, but how to do other arithmetic?
  - how to subtract? how to represent negative numbers?
  - how to multiply?
  - how to divide? how to represent fractional numbers?



# Converting decimal to binary

- Binary to decimal is easy. Powers of two
- Decimal to binary is harder.
- Successive division by 2.
- Then read the remainders from bottom to top:
  - example: what is 307 in binary?

$$\begin{aligned} 100110011 &= 256 + 32 + 16 + 2 + \\ &= 307 \end{aligned}$$

$$307 \div 2 = 153 \text{ r } 1$$

$$153 \div 2 = 76 \text{ r } 1$$

$$76 \div 2 = 38 \text{ r } 0$$

$$38 \div 2 = 19 \text{ r } 0$$

$$19 \div 2 = 9 \text{ r } 1$$

$$9 \div 2 = 4 \text{ r } 1$$

$$4 \div 2 = 2 \text{ r } 0$$

$$2 \div 2 = 1 \text{ r } 0$$

$$1 \div 2 = 0 \text{ r } 1$$

# Converting decimal to binary

- convert  $41_{10}$  to binary

$$41 \div 2 = 20 \text{ r } 1$$

$$20 \div 2 = 10 \text{ r } 0$$

$$10 \div 2 = 5 \text{ r } 0$$

$$5 \div 2 = 2 \text{ r } 1$$

$$2 \div 2 = 1 \text{ r } 0$$

$$1 \div 2 = 1 \text{ r } 1$$

101001

confirm:  $32 + 8 + 1 = 41$

Practice: pick a random number between 0 and 100 and convert it. Then confirm.

# Some Terminology

- MSB: Most Significant Bit
  - The leftmost bit of a stream
- LSB: Least Significant Bit
  - The rightmost bit of a stream
- e.g. 10010100
  - MSB is 1, corresponding to  $1 \times 2^7$
  - LSB is 0, corresponding to  $0 \times 2^0$

# Binary arithmetic: remember the Full Adder

- Addition: Just like high school
  - Line up similar place values
  - Any result bigger than will fit in the column results in a carry into the next column
  - decimal:  $5+7=12 \rightarrow 2$  with 1 carried to the 10s column
  - binary:  $1+1=10 \rightarrow 0$  with 1 carried to the 2s column

(1) (1) (1) (1) *carries*

$$\begin{array}{r} 1015 \\ + 1117 \\ \hline 1102 \end{array}$$

# Binary arithmetic: Subtraction

- Subtraction: Just like addition
  - Line up similar place values
  - Borrow from the next column if necessary

Diagram illustrating binary subtraction:  $1011 - 111$ . The minuend is 1011 and the subtrahend is 111. The result is 101. Borrow arrows are shown: from the 4s column to the 3s column, from the 3s column to the 2s column, and from the 2s column to the 1s column. The borrowed values are labeled as (10), (10), and (1) respectively.

$$\begin{array}{r} 1011 \\ - 111 \\ \hline 101 \end{array}$$

Diagram illustrating decimal subtraction:  $12 - 7$ . The minuend is 12 and the subtrahend is 7. The result is 5. A borrow arrow is shown from the 2s column to the 1s column, labeled (10).

$$\begin{array}{r} 12 \\ - 7 \\ \hline 5 \end{array}$$

borrows

- 1s column needs to borrow, but nothing in 2s column, so borrow from 4s column.

# Subtraction: Bitslice Truth Table $D = X - Y$

- (in this slide + is plus, not OR)
- $B_{in}$  means a column to the right has borrowed from this column,
  - so subtract 1 from  $X - Y$
- $B_{out}$  is a request to borrow from the *next* column to the left
  - so add 2 (binary 10) to  $X - Y$
- if  $X < (Y + B_{in})$  then borrow from the next column ( $B_{out} = 1$ ).
- then  $D = 2 \times B_{out} + X - Y - B_{in}$

X	Y	$B_{in}$	$B_{out}$	D
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	1	0
1	0	0	0	1
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1



# Subtraction: the bitslice functions

- $D = X \oplus Y \oplus B_{in},$
- $B_{out} = \bar{X}\bar{Y}B_{in} + \bar{X}Y\bar{B}_{in} + \bar{X}YB_{in} + XYB_{in}$   
 $= \bar{X}(Y \oplus B_{in}) + YB_{in}$ 
  - ➔ exercise: prove with k-maps
  - ➔ does it look familiar?
- But what happens if a borrow fails (i.e. what if  $X < Y$ )?
- if  $X < Y$ , the result will be negative
  - What does that mean in binary?
  - Tangent time...

# Number Representation in Binary

- Recall unsigned representation:
  - Each bit means ' $+a \times 2^n$ '
  - Always positive, since  $a$  can only be 0 or 1
- What about negative numbers?
  - We need *signed numbers* for subtraction.
- 3 common signed representation options, in order from obvious to useful:
  - ▶ Sign-magnitude
  - ▶ Complement
  - ▶ 2's complement

# Sign-Magnitude

- In decimal, we use extra symbols for the sign
  - ▶ ' - ' means negative, ' + ' means positive
- In binary, we can't just add extra symbols
  - only have "0" and "1"
  - So use an extra bit for the sign
  - Adding 0 at the beginning should not change the value
    - ▶ so 0 means positive, and 1 means negative.
- For example,
  - ▶  $0101_2 = +5_{10}$ , and  $1010_2 = -2_{10}$

# Subtraction with Sign-Magnitude

1. Check sign of both operands
2. Perform appropriate math
  - e.g.:  $-x - y$  would be treated as  $-(x + y)$ ,
  - add  $x$  to  $y$ , then add "1" to make the result negative.
- Lots of logic to design
  - Check sign,
  - Logic for each sign combination and operation
    - ▶ 4 possibilities for add, 4 for subtract

# Complement

- if  $X$  is the binary encoding of the number, let  $\bar{X}$  be the negative version of that
  - Negating is the equivalent inverting, seems intuitive
  - Need very different representations for negative and positive:
    - ▶  $5 = 0101$
    - ▶  $-5 = 1010$ 
      - Each bit no longer corresponds to  $' +a \times 2^n '$
      - Need a second step to figure out value

# 2's Complement

- Binary version of the "Radix Complement"
  - Subtract from the next higher power of the radix
- We'll do 10's complement first to get the feel.
- To form the 10's complement:
  - Subtract from the next higher power of 10
  - e.g.: 10's complement of 209 is **1000** – 209 = 791
  - so 791 means -209 in 10's complement
- The goal is to be able to subtract by adding
  - For example,  $a - b = a + (-b)$



# 10's Complement subtraction by adding

- Use 10's complement for subtraction:

$$315 - 209$$

$$= 315 + 1000 - 209 - 1000$$

- ▶  $1000 - 209 = 791$  is ten's complement for  $-209$
- ▶ the extra " $-1000$ " maintains the numerical value

$$= 315 + 791 - 1000$$

$$= 1106 - 1000$$

$$= 106, \text{ which is the correct answer.}$$

- Adding is easy, and dropping the extra  $1000$  is easy.
- Is finding 791 easy?

# Easily find the 10's complement

- to find the simple complement, subtract each bit from the biggest digit in the representation
  - in base 10, that value is 9
  - also called 9's complement
    - ▶ The 9's complement of 209 would be 790
- The 10's complement is just the 9's complement, plus 1
- So finding the 10's complement is easy, adding is easy, and dropping the next higher power of 10 is easy, so we can subtract without subtracting



# Now, in Binary

- Subtract from next higher power of 2.  
e.g.  $43_{10} = 0101011_2$ .
  - the two's complement representation of -43 is:
    - ▶  $10000000 - 0101011 = 1010101$
- Can we form it without using subtraction, using the trick from 10's complement?
- Look at the subtraction table again:

The diagram illustrates the two's complement calculation for -43. It shows the subtraction of 43 (0101011) from 10000000. The first row, 10101010, is crossed out with a blue diagonal line. Above it, a series of blue arrows point right, each labeled with a '1', indicating the carry propagation from the first zero to the leftmost '1'. The result of the subtraction, 1010101, is shown below a horizontal line.

$$\begin{array}{r} \cancel{10101010} \\ \phantom{1}10000000 \\ - \phantom{1}0101011 \\ \hline 1010101 \end{array}$$

# Forming the 2's complement

$$X - Y = 10000000 - 0101011$$

- Except for the MSB, the bits of  $X$  are always 0, which means repeated borrows.
- If we could make it so that  $X$  is always 1, there would be no borrows, implying  $D = Y'$
- Notice that  $1000000 - 1 = 111111$

X	Y	B <sub>in</sub>	B <sub>out</sub>	D
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	1	0
1	0	0	0	1
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

# Forming the 2's complement

- 2's complement of  $43_{10}$   
 $10000000 - 0101011 = 1010101$   
 $(10000000 - 1) + 1 - 0101011 = 1010101$   
 $1111111 - 0101011 + 1 = 1010101$   
 $(0101011)' + 1 = 1010101$
- So, to form 2's complement, take the logical complement and add 1.
  - ▶ (just like in the 10's complement)
  - No subtraction necessary!

# 2's complement for subtraction

- e.g.:  $50_{10} - 43_{10} = 0110010 - 0101011 = 0111 = 7_{10}$
- Using the 2's complement idea:  
$$\begin{array}{rcl} & 0110010 & - 0101011 \\ = & 0110010 & + \textcolor{blue}{1010101} - \textcolor{red}{1000000} \\ = & 1000111 & - \textcolor{red}{1000000} \\ = & 0111 & \end{array}$$

*complement and add 1*
- We still have to subtract out the next higher power of 2 to maintain numerical equivalence.

# 2's complement representation

- To make this idea workable, we need
  1. Some way to identify positive or negative numbers
  2. Some way to easily subtract out the next higher power of 2.
- Solution:
  1. Add another bit, same as in signed-magnitude, in the MSB location
  2. This bit will correspond to  $-a \times 2^k$
  3. All other bits correspond to  $+a \times 2^k$

# 2's complement representation

- e.g.: 7 bit representation:  $-2^6 + 2^5 + 2^4 + 2^3 + 2^2 + 2^1 + 2^0$ 
  - ▶ For small enough positive numbers:  
 $0010101 = 16 + 4 + 1 = 21$
  - ▶ For negative numbers:  
$$\begin{aligned} -43 &= -1000000 + (1000000 - 101011) \\ &= -1000000 + 0010101 \\ &= -2^6 + 2^4 + 2^2 + 2^0 = -64 + 16 + 4 + 1 = -43 \end{aligned}$$
- So the complete representation is **1**010101 and can be formed simply by inverting the positive and adding 1:
  - $43 = 0101011 \rightarrow -43 = 1010100 + 1 = 1010101$

# Limits of 7-bit 2's complement

- 0000000 is still  $0_{10}$ . That's good.
- The largest positive number is when the negative bit is 0, and all positive bits are 1:
  - ▶ 0111111, which is  $63_{10}$ .
- The largest negative number is when the negative bit is 1, and all positive bits are 0:
  - ▶ 1000000, which is  $-64_{10}$ .
- All 1's equals  $-1$ :  $1111111 = -64 + 63 = -1$



# Range of 2's complement representation


- Since  $|-64| > |63|$ ,
  - ▶ All positive numbers have  $\text{MSB} = 0$
  - ▶ All negative numbers have  $\text{MSB} = 1$
  - ▶ So we can interpret the  $\text{MSB}$  as a sign bit!
- For 7 bits, range is  $-64..+63$
- In general, for  $n$  bits, range is
  - ▶  $-2^{n-1}$  to  $2^{n-1}-1$



# Confirmation of 2's complement representation

- Positive numbers now require a leading zero.
  - e.g.  $0111 = +7$ ,  $111 = -1$
- The size of the representation is important
  - The MSB is negative and all other bits are positive
- $-(-N)$  should equal  $+N$
- e.g.:  $-(-17_{10})$ 
  - ▶  $+17 = 16+1 = 010001$
  - ▶  $-17 = 101110+1 = 101111$
  - ▶  $-(-17) = 010000+1 = 010001$

*hooray!  
wait, what?*

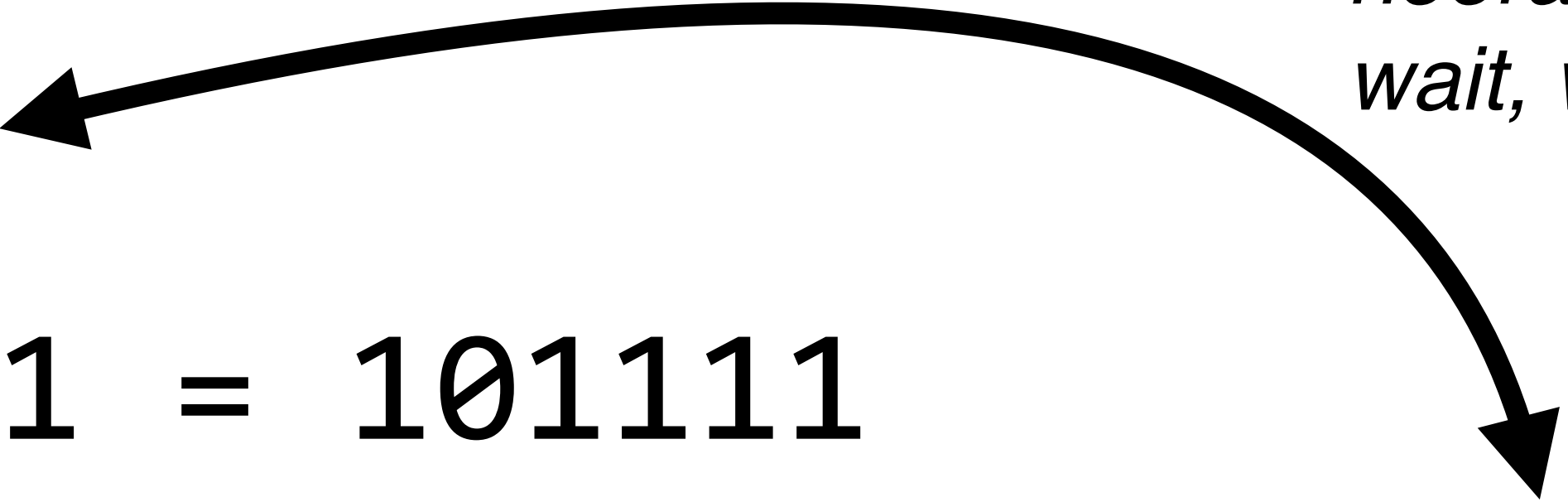

# The wierness of 2's complement

- If you flip the bits and add 1 to form the negative, you should have to subtract the bits before you flip, to undo that change.
- but flipping the bits and adding 1, twice, gets you back to the same value you started with
  - So for any  $X$ ,  $\overline{\overline{X}}+1 = (X-1)'$
- Note: 2's complement is both a noun (the name of our representation) and a verb (to flip the bits and add 1)
- Remember, positive numbers are unchanged

# 2's complement: doing math

- 2's complement should allow us to subtract by adding (that was the goal)
- Try a bit-by-bit addition of a negative number
  - e.g.  $50 - 43 = 50 + (-43) = 7$

		$-2^6$	$2^5$	$2^4$	$2^3$	$2^2$	$2^1$	$2^0$	
50		1	10	11	1	0	0	1	0
-43	+		1	0	1	0	1	0	1
<hr/>									
7	(1)	0	0	0	0	1	1	1	

- Note: Ignore the final carry out for the time being

# Some Practice

- Convert the following to 2's complement (use a 7-bit representation):

25 =

-11 =

- Do the following math using 2's complement

25 + 11 =

25 - 11 =

11 - 25 =


# 2's complement add/sub circuit

- To add, use full adder
- To subtract, add the complement + 1

$S = 0: Q = A + B$

$S = 1: Q = A - B$

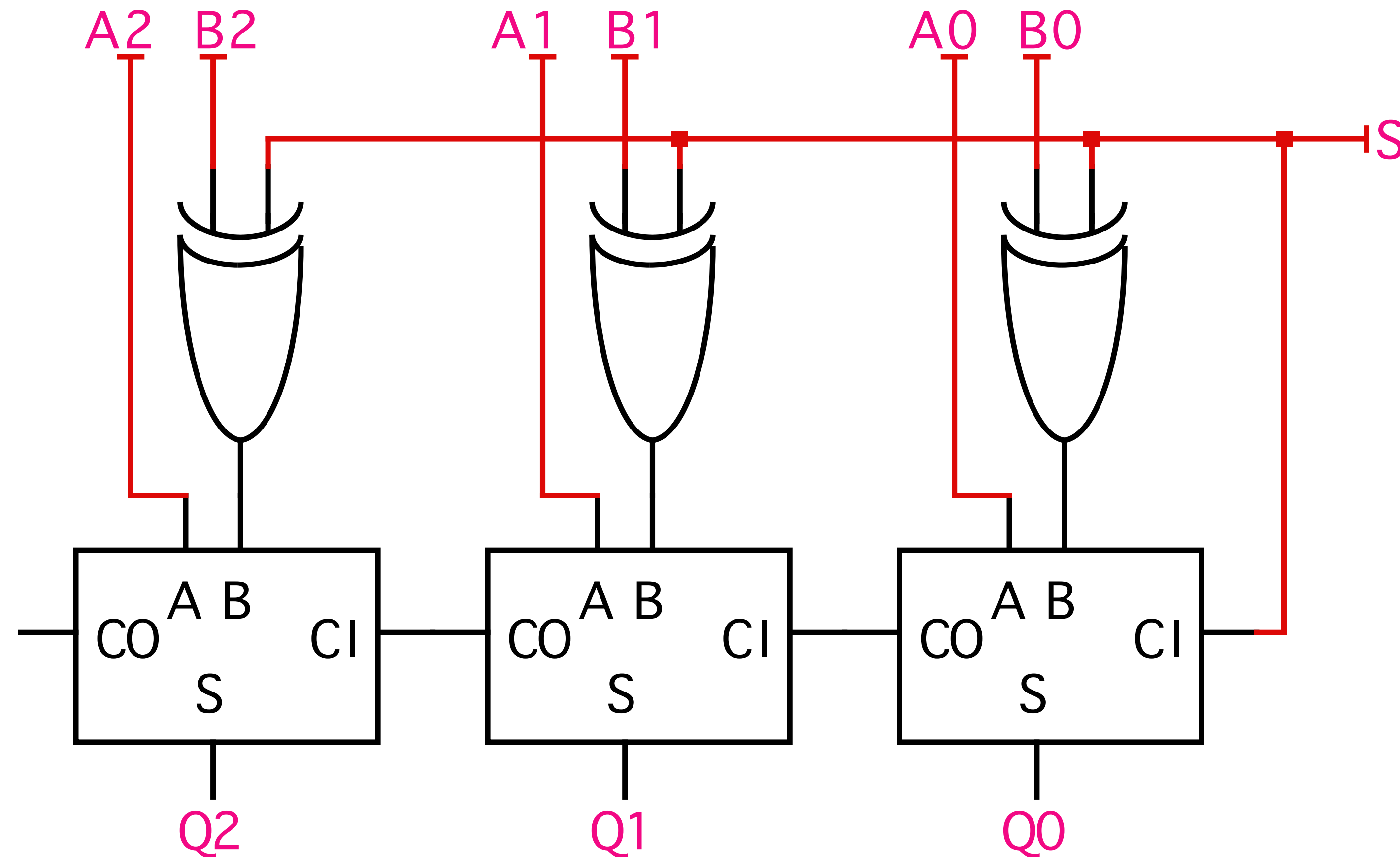XOR is used as a controlled complement (recall the truth table).  
 $C_i = S$  adds the required "1" when subtracting.



# Overflow

- Using a 7-bit representation, consider  $50 + 21 = 71$

	$-2^6$	$2^5$	$2^4$	$2^3$	$2^2$	$2^1$	$2^0$
50	1	0	1	1	0	0	1
+21		0	0	1	0	1	0
<hr/> 71	<hr/> 1	<hr/> 0	<hr/> 0	<hr/> 0	<hr/> 1	<hr/> 1	<hr/> 1

- The result will be wrongly interpreted as -57
- Carry from the  $+2^5$  column into the  $-2^6$  column.
  - Doesn't make sense. columns mean different things
- Arithmetic Overflow:** The result of an operation is too large for the representation.
- NOT THE SAME AS carry out.

# Overflow

- Consider  $-50 - 21 = -71$

	$-2^6$	$2^5$	$2^4$	$2^3$	$2^2$	$2^1$	$2^0$
$-50$	1	1	0	10	11	11	1 0
$-21$		1	1	0	1	0	1 1
<hr/>	<hr/>	<hr/>	<hr/>	<hr/>	<hr/>	<hr/>	<hr/>
$-71$	(1)	0	1	1	1	0	0 1

- Ignoring the final carry-out, as before.
- The result will be interpreted as +57.
- This is also arithmetic overflow.
  - in this case, carrying out of the  $-2^6$  column into who knows what?




# Overflow Detection

- It is important to know when overflow occurs
  - We can design other hardware to handle it later.
- Seems to occur when carrying into or out of the MSB
  - MSB Column is negative, carry-in to it would be positive.
  - but if we carry in AND carry out:
    - ▶ the representation is correct again
      - ◎ (recall 50 – 43)
    - ▶ although final carry out is still wrong.


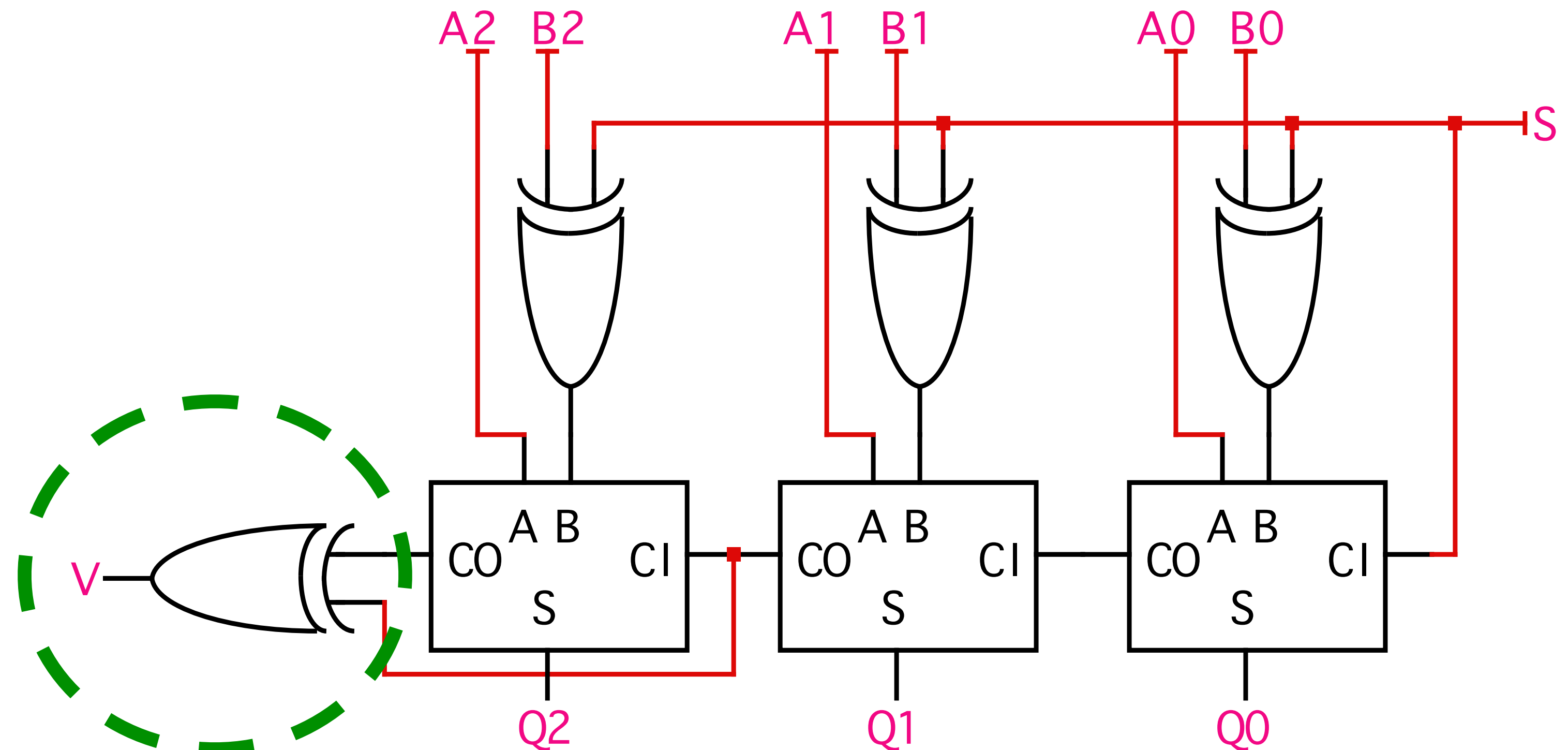
# Overflow Detection

- In general: if we carry in but don't carry out, or if we carry out but don't carry in, there's a problem.
- Overflow when  $C_i=1$  and  $C_o=0$ , or  $C_i=0$  and  $C_o=1$
- $C_i \neq C_o$ , which is the same as  $C_i \oplus C_o$
- Final circuit:



# Representation Size

- Overflow is a consequence of representation size
  - If the answer can't fit, you get overflow.
- Can we change the size of the representation?
  - make a bigger 2's complement that would fit?
- eg: Start with a 4-bit representation:  $-2^3 + 2^2 + 2^1 + 2^0$ 
  - ▶  $1000 = -8$ ,  $0111 = +7$ ,  $1111 = -1$
- To switch to a 5-bit representation:  $-2^4 + 2^3 + 2^2 + 2^1 + 2^0$ 
  - ▶  $-8 = -(01000) = 10111 + 1 = 11000$
  - ▶  $+7 = 00111$

# Sign Extension

- We can add lots of 0s to the left of a positive number without changing its value
- Similarity, we can add lots of 1s to the left of a two's complement negative number without changing its value
  - ▶ subtract  $2^n$  for the new negative MSB,
  - ▶  $2^{(n-1)}$  was the negative MSB, but is now positive
  - ▶ so we must add  $2^{(n-1)}$  back to the value, twice
  - ▶ since  $2^n = 2^{(n-1)} + 2^{(n-1)}$ , the value is unchanged

101 = 1101 = 11101 = 1111111101

010 = 0010 = 00010 = 00000000010


$- 2^4 + 2^3 + 2^2 + 2^1 + 2^0$

$- 2^5 + 2^4 + 2^3 + 2^2 + 2^1 + 2^0$

# Faster addition

- Recall: full adder has big gate delay
- Also called "Ripple Carry" adder
  - Carry ripples from one adder to the next
  - Total circuit delay depends on the word size.
  - 64 bit adder has **64 full-adders** worth of gate delay.
    - ▶ we know any circuit can be built with at most 3 levels of gate delay
- Carry lookahead
  - To design some logic so adder can be faster
  - Recognize relationship between  $C_i$  and  $C_o$

# Ripple-carry adder

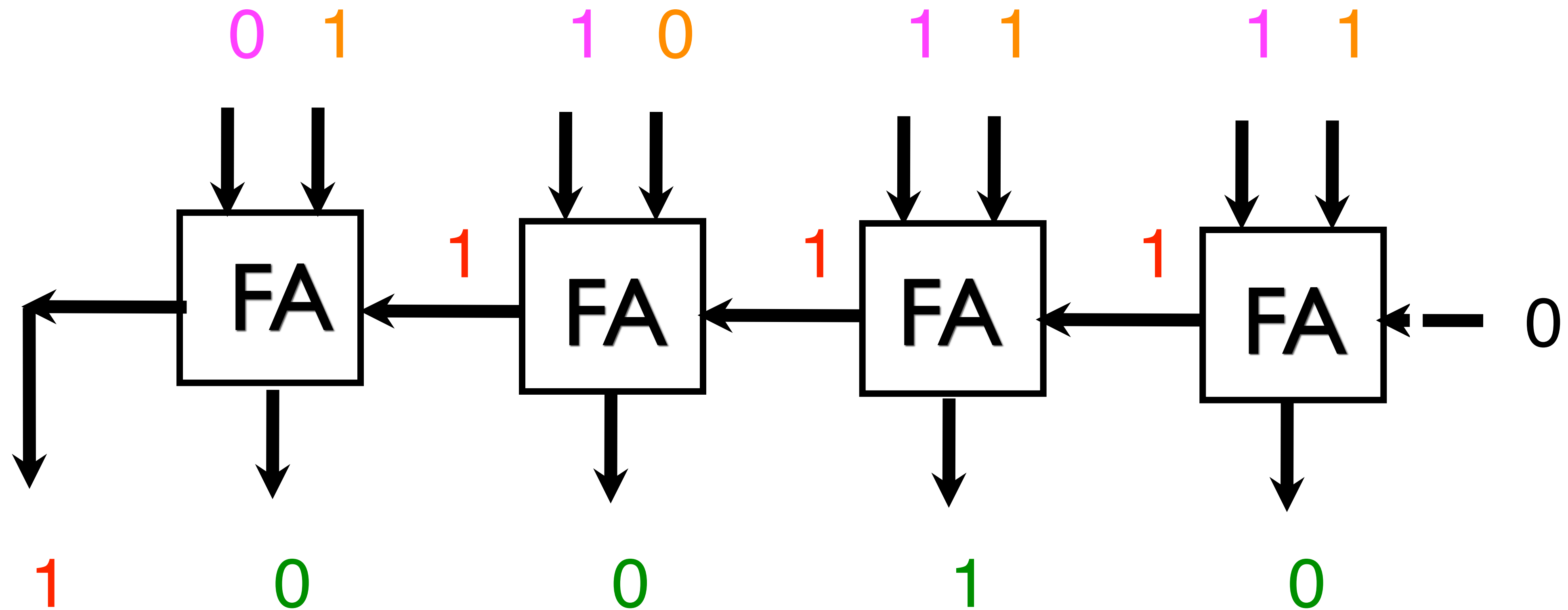

# Recall full adder expressions

$$s_i = x_i \oplus y_i \oplus c_i \quad co_i = x_i y_i + x_i c_i + y_i c_i$$

- Carry-out is the carry-in for the next full adder

$$co_i = c_{i+1} \quad \text{So we'll just use "c"}$$

$$\begin{aligned} c_{i+1} &= x_i y_i + x_i c_i + y_i c_i \\ &= x_i y_i + (x_i + y_i) c_i \end{aligned}$$

- Both  $x_i y_i$  and  $(x_i + y_i)$  take only 1 gate delay.
- $c_i$  is what takes time so let's get rid of it.

# Carry Look-ahead

- Starting from the LSB

$$c_1 = x_0 y_0 + (x_0 + y_0) c_0$$

$$c_2 = x_1 y_1 + (x_1 + y_1) c_1 \quad (\text{then replace } c_1 \text{ as above})$$

$$c_2 = x_1 y_1 + (x_1 + y_1) [x_0 y_0 + (x_0 + y_0) c_0]$$

- next do  $c_3$ . This will get big quickly.
- Let's rename parts of these expressions
  - $x_i y_i$  = Carry Generate ( $G_i$ )
  - $x_i + y_i$  = Carry Propagate ( $P_i$ )
- These are both available in 2 gate delays.
  - Neither depends on the carry-in.
- Why these names...



# Carry Look-ahead

- *Carry Generate*: Start a carry regardless of the other inputs.
- *Carry Propagate*: If a carry comes in, pass it along, but don't generate a new carry.
- Have a look at the functions, and this makes sense:

$$C_{i+1} = x_i y_i + (x_i + y_i) C_i$$

$x_i y_i$ : if  $x_i$  and  $y_i$  are both 1, there would be a carry out of that bitslice regardless of the other inputs.

$x_i + y_i$ : if  $x_i$  or  $y_i$  are 1, there would be a carry out of that bitslice only if there was a carry in to that bitslice.



# Carry Look-ahead

- Using the generate and propagate functions:

$$c_1 = g_0 + p_0 c_0$$


$$\begin{aligned} c_2 &= g_1 + p_1 c_1 = g_1 + p_1 (g_0 + p_0 c_0) \\ &= g_1 + p_1 g_0 + p_1 p_0 c_0 \end{aligned}$$

$$c_{i+1} = g_i + p_i g_{i-1} + p_i p_{i-1} g_{i-2} + \dots + p_i p_{i-1} \dots p_0 c_0$$


- This will require *lots* more hardware, but
- Guaranteed to execute in 4 gate delays.
  - $p_i$  and  $g_i$  are generated in one gate delay
  - $c_i$  takes two gate delays from  $p_i$  and  $g_i$
  - sum takes one more delay
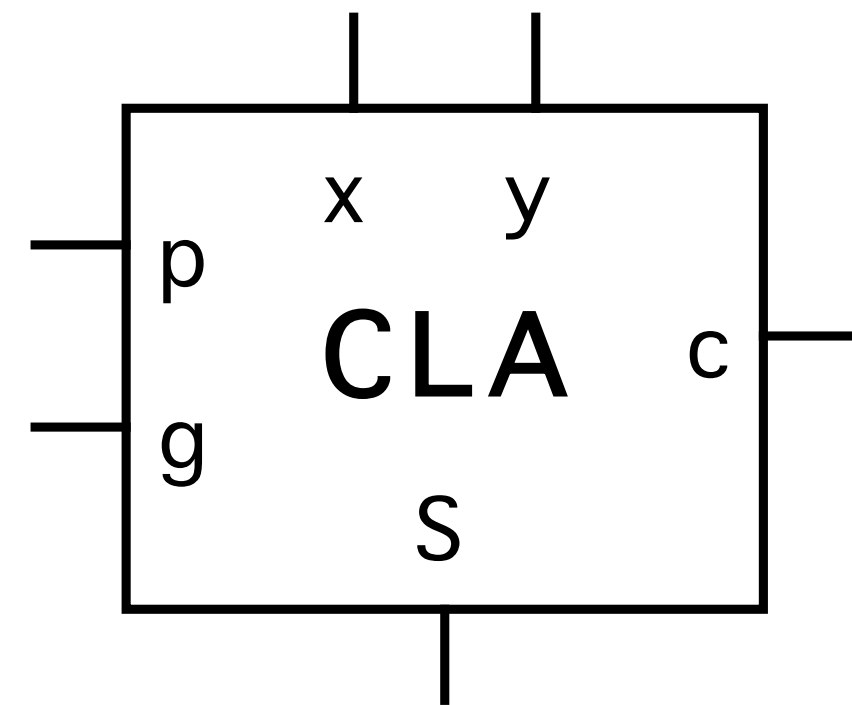
# CLA Hardware

- Modify the Full Adder:
  - output  $p_i$  and  $g_i$ , not  $c_i$



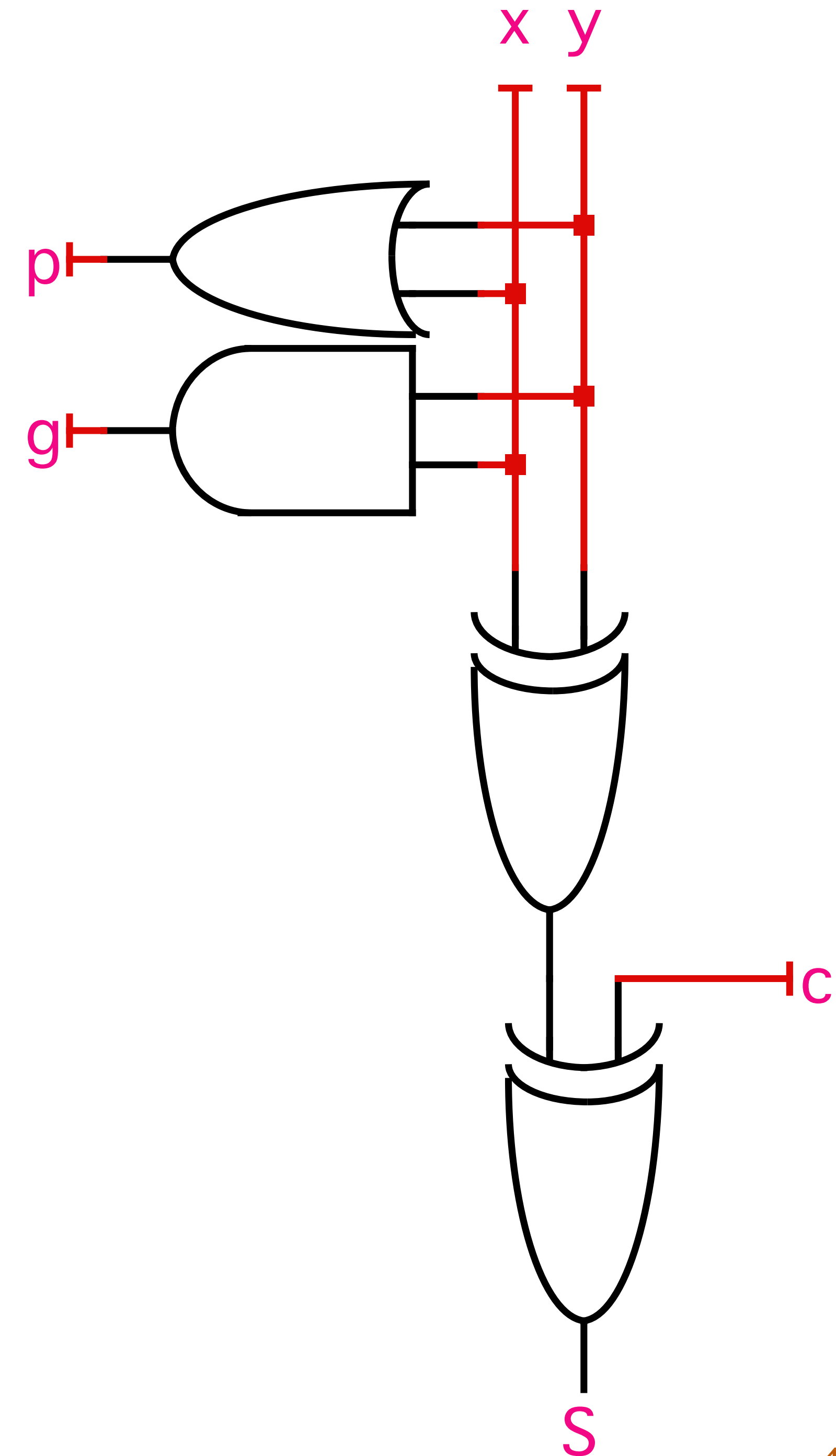
- Connect them to create a 4-bit carry-look ahead adder.
  - Lots of additional logic is still required to work with the new  $P$  and  $G$  signals



# How do we generate c for each bitslice?

- Carry in at bitslice  $i$  is true if there is a generate from  $i-1$ , or a propagate passing along a carry from a previous slice
- for each bitslice,  $c_i = g_i + p_i c_{i-1}$
- The hardware is constructed recursively, duplicating and building on the logic for calculating carry from generation and propagation from each previous bitslice
- 64 bit adder will have hundreds of gates, thousands of inputs
  - *Trade complexity for speed*

# 4-bit CLA

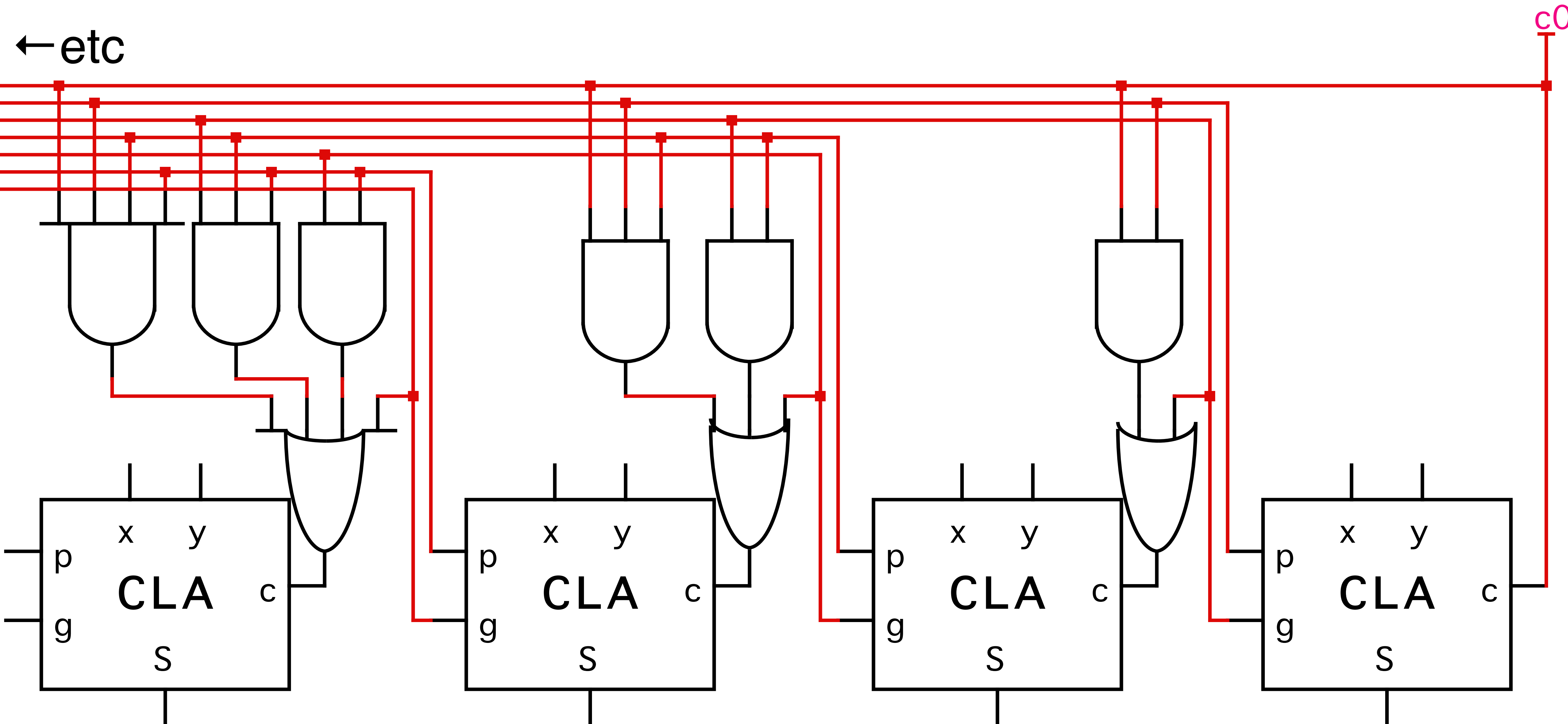


# ALU: Putting it all together

- Building each individual component of the ALU is done
- To put it all together, we just need multiplexers
  - Generate all possible answers
  - use MUX to choose which answer we will use
  - control signals to ALU are used to select output
- Flags are output signals that give useful information
  - was the result zero? was the result negative? was there overflow?
- Add, subtract, logic, and shifting are all useful

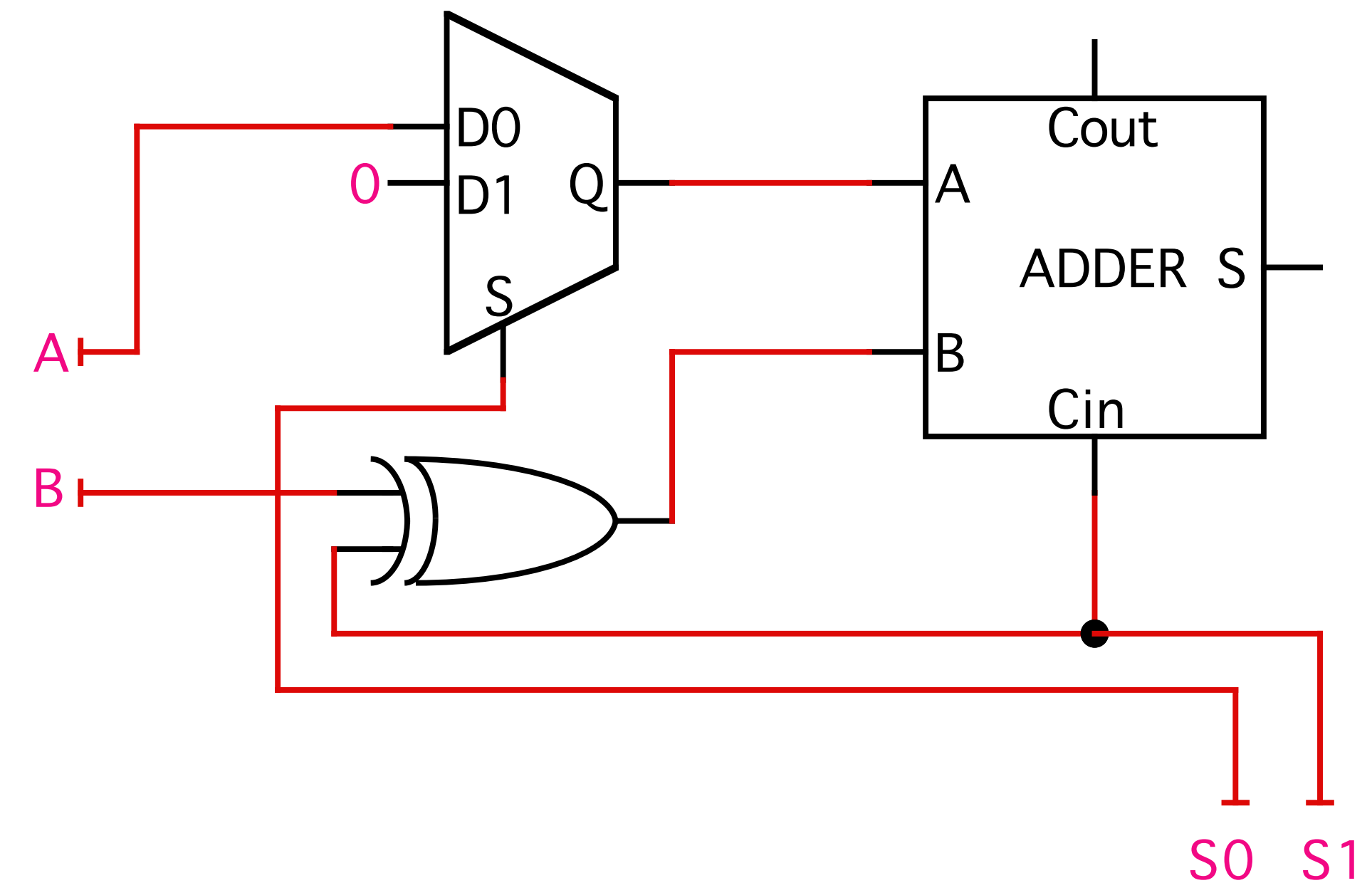
# ALU: Arithmetic

- Desired functions: add, subtract, negative, pass-through
  - or other functions
- Start with adder
- add XOR to B to allow  $\pm B$
- Add MUX to A to allow  $A \pm B$  or  $0 \pm B$
- 2 control signals needed
  - ▶ S0:  $S/\bar{A}$
  - ▶ S1:  $A=0$


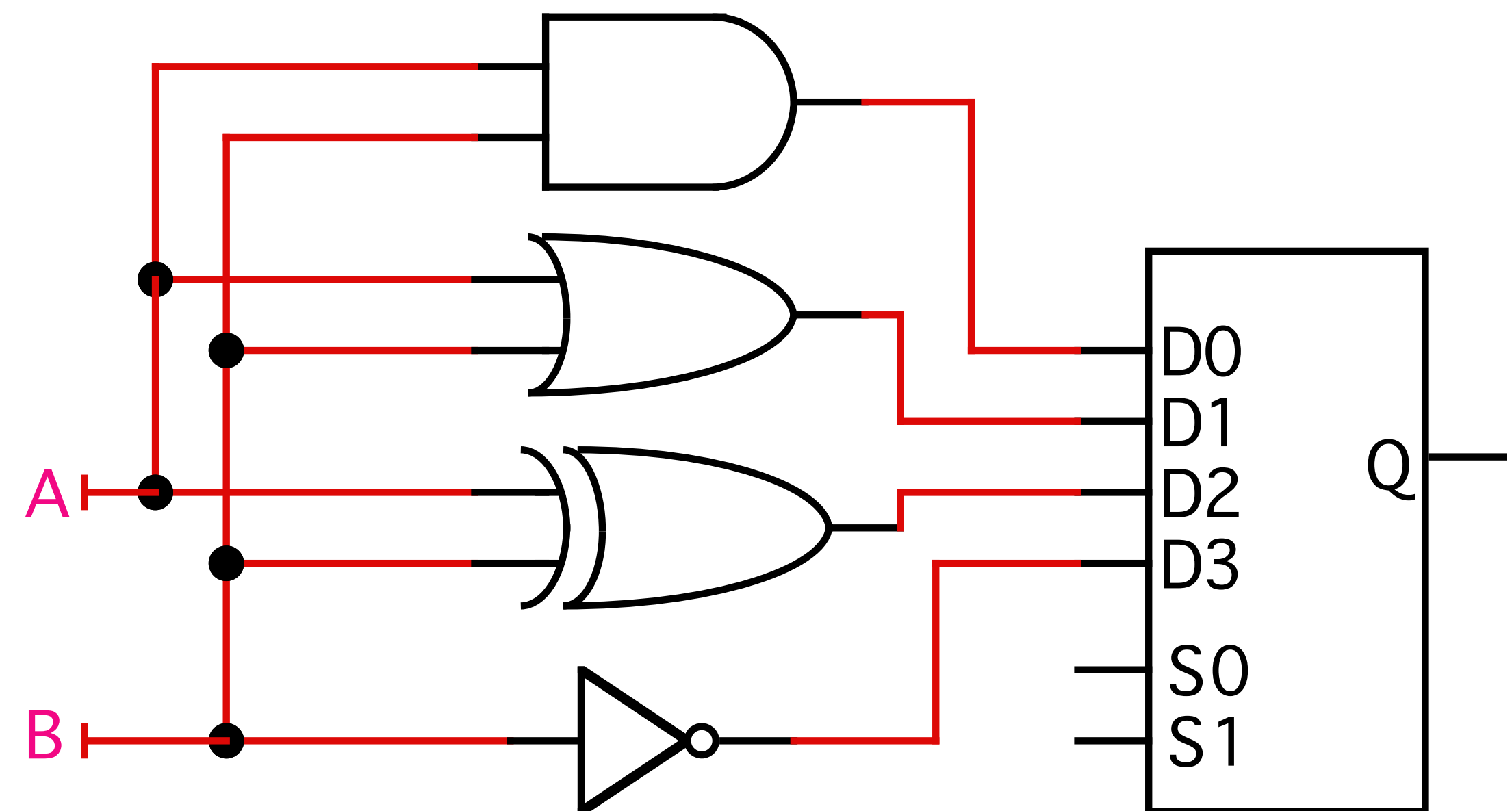
# ALU: Logic

- Pick desired logic functions
  - AND, OR, NOT, XOR
- Select between them with a MUX
  - Again, two control signals
  - Can use the same 2 signals as for Arithmetic
- Select either Arithmetic or Logic with a final MUX and a third control signal (S2)






# ALU: FLAGS


- Output signals that indicate certain conditions
- Typical flags: NZVC

- ▶  $N = \text{Negative} = \text{MSB of output } (F_{n-1})$
- ▶  $Z = \text{Zero} = \text{NOR of output } (F_{n-1} + F_{n-2} + \dots + F_0)'$
- ▶  $V = \text{Overflow} = C_{n-1} \oplus C_{n-2}$
- ▶  $C = \text{Carry} = C_{n-1}$

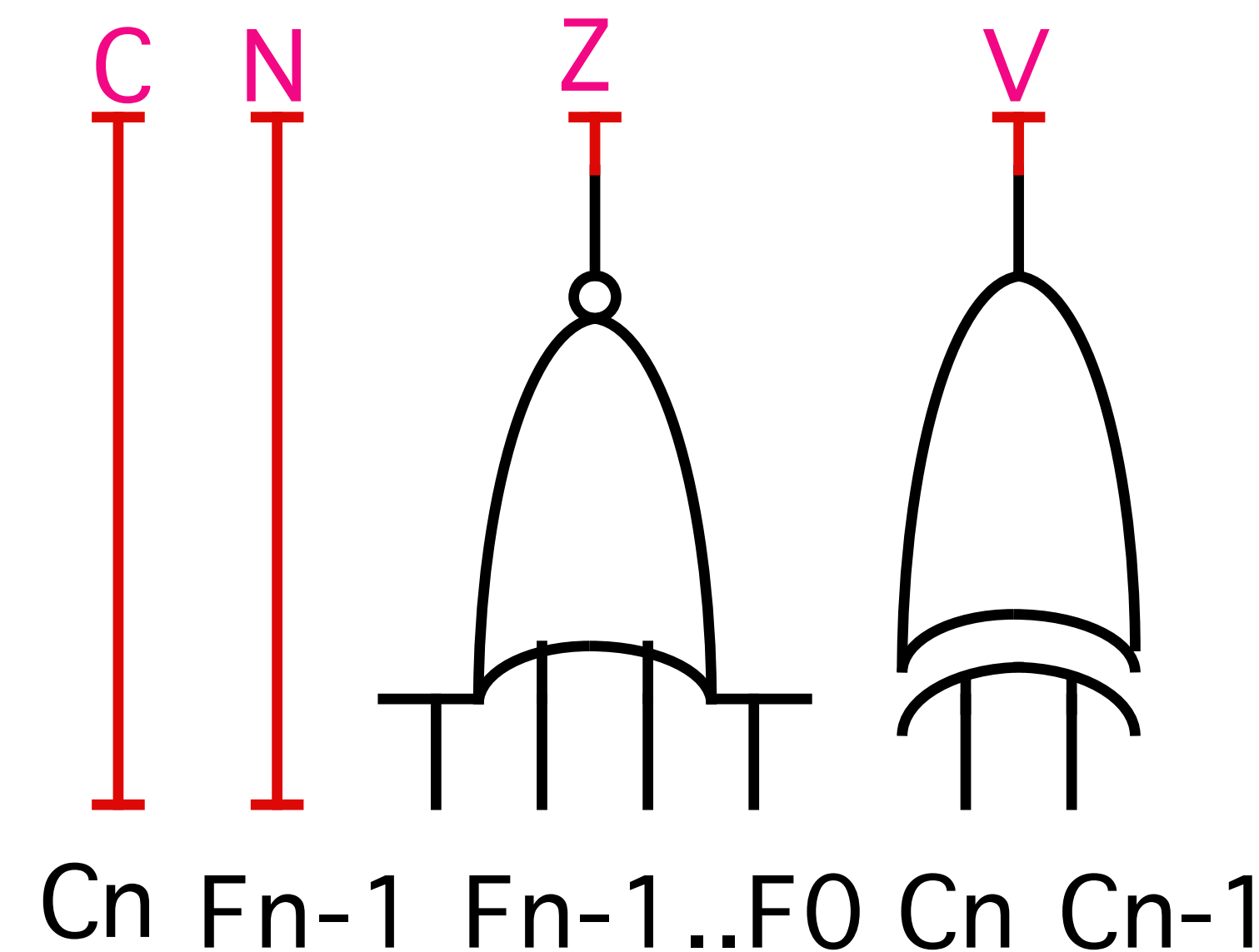- NOTE: different ALU will have different functions, different flags
- NOTE: ALU is entirely combinational



# Complete ALU and function table

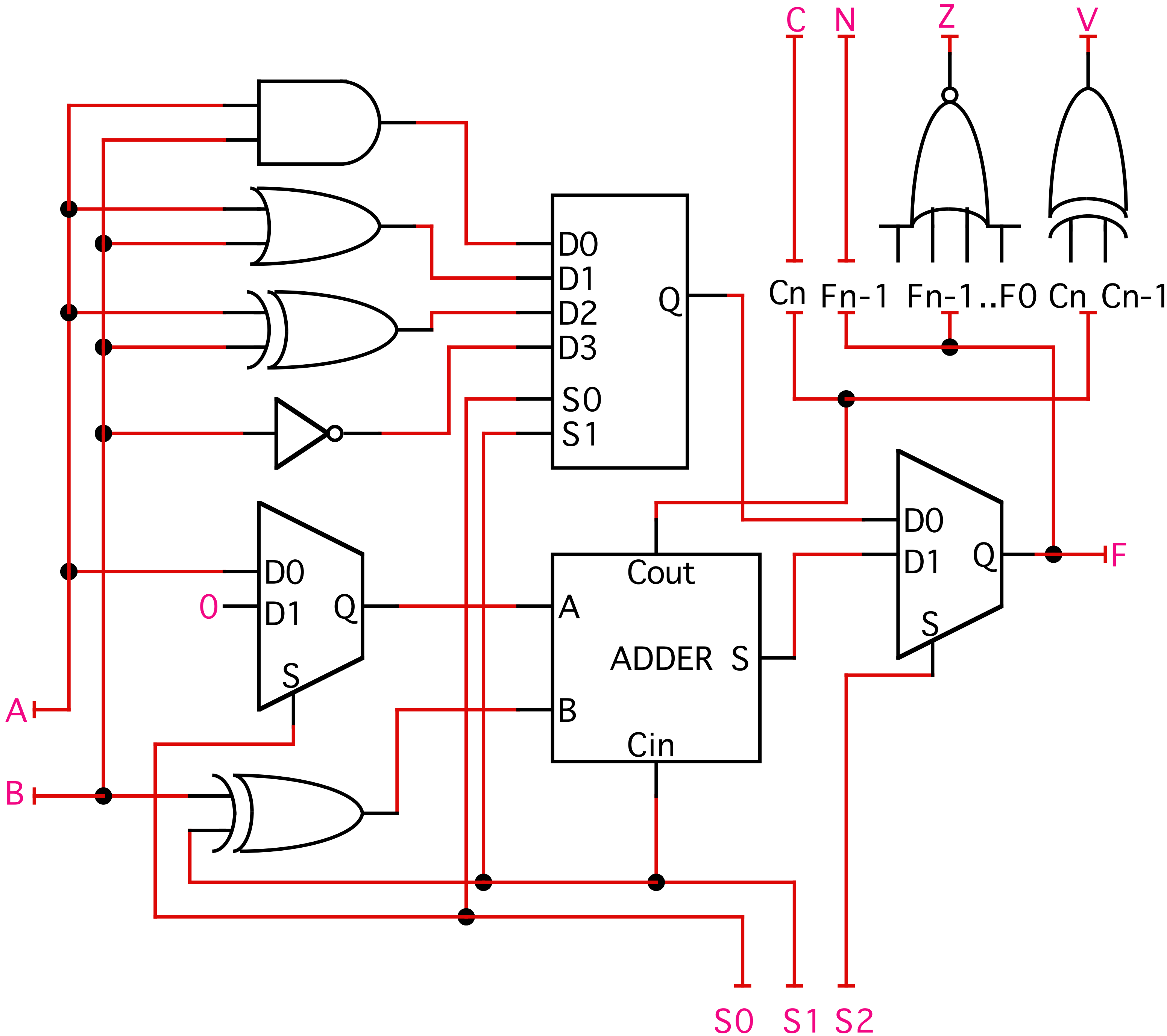

S2	S1	S0	F
0	0	0	AND
0	0	1	OR
0	1	0	XOR
0	1	1	$\overline{B}$
1	0	0	A+B
1	0	1	+B
1	1	0	A-B
1	1	1	-B

# Sequential Math

- ALU is fine for combinational arithmetic
- Some arithmetic will require multiple steps, decision making, state machines etc
  - ▶ Multiplication and Division, to start
- These could be done combinational, since the answer is the same for the same input
  - but the logic would be very large and complex
  - In practice, sometimes done with look-up tables to speed up the process
- Other common sequential math: graphics processing

# Sequential Math: Binary Multiplication

Recall grade 3 math. eg  $14 \times 10 = 140$

$$\begin{array}{r}
 1110 \\
 \times 1010 \\
 \hline
 0000 \\
 1110\phantom{0} \\
 0000\phantom{00} \\
 1110\phantom{000} \\
 \hline
 10001100
 \end{array}$$

$$\begin{aligned}
 &= 0 \times 1110 \times 2^0 \\
 &= 1 \times 1110 \times 2^1 \\
 &= 0 \times 1110 \times 2^2 \\
 &= 1 \times 1110 \times 2^3 \\
 &= 140
 \end{aligned}$$

(Multiplicand)

(Multiplier)

(Partial Products)

(Product)


Note: the trailing zeros are usually implied.

Note: assume positive numbers.


# Binary Multiplication

- You've seen this in the lab, I think
- Registers, with shift
- Adding with carry
- Repeated shift and add, accumulating result
- Shifting a 0 into the register will maintain the partial products
- Add or not add the multiplicand, based on the current bit of the multiplier
- We'll go into more detail, build a couple variants

# Binary multiply implementation

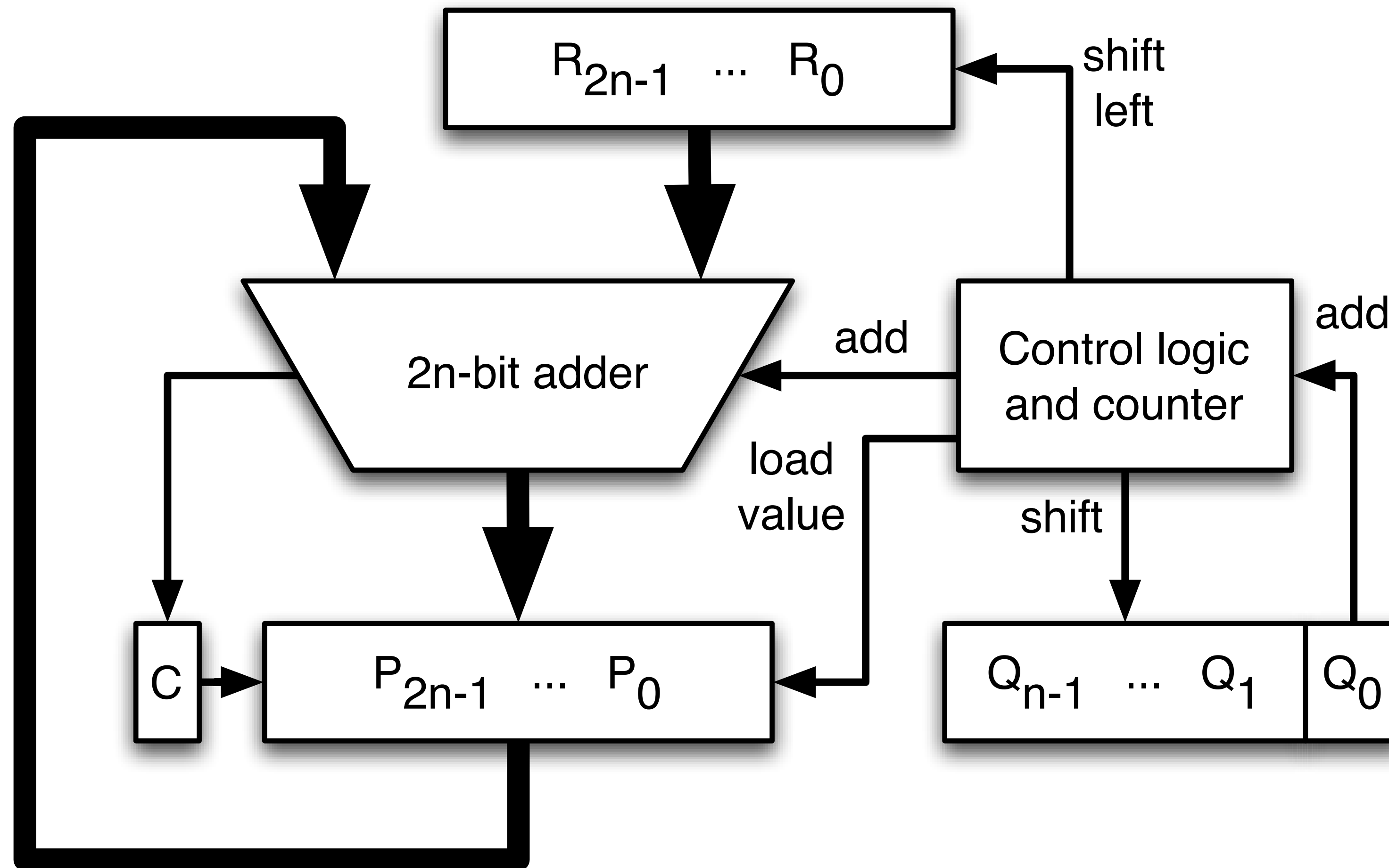

# Binary multiply flowchart

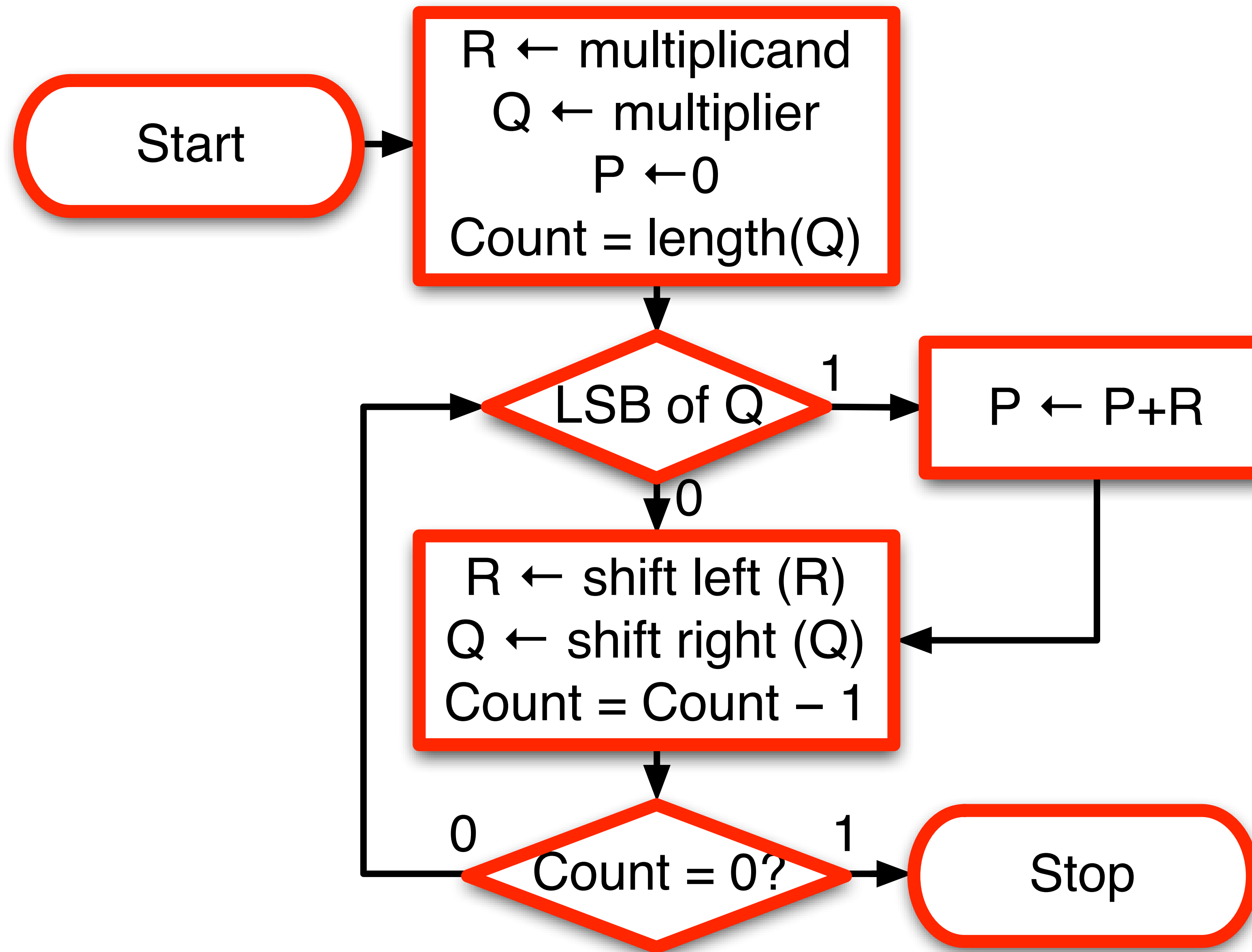



# Binary multiply example

- e.g.:  $14 \times 10 = 140$       Step by step:


count	R	Q	P
4	1110	1 0 1 0	0
3	11100	1 0 1	11100
2	111000	1 0	11100
1	1110000	1	10001100
0	Done. P=10001100		

# Binary multiply algorithm

- Use a down-counter to decide when done
  - Start with  $c = \text{length}(Q)$
  - done when  $c = 0$
- Store  $Q$ ,  $R$  and  $P$  in shift registers
  - $\text{size}(Q) = \text{number of bits in } Q$
  - $\text{size}(R) = 2 \times \text{size}(Q)$  (room for left shifts)
  - $\text{size}(P) = 2 \times \text{size}(Q)$
- Other logic to control the circuit
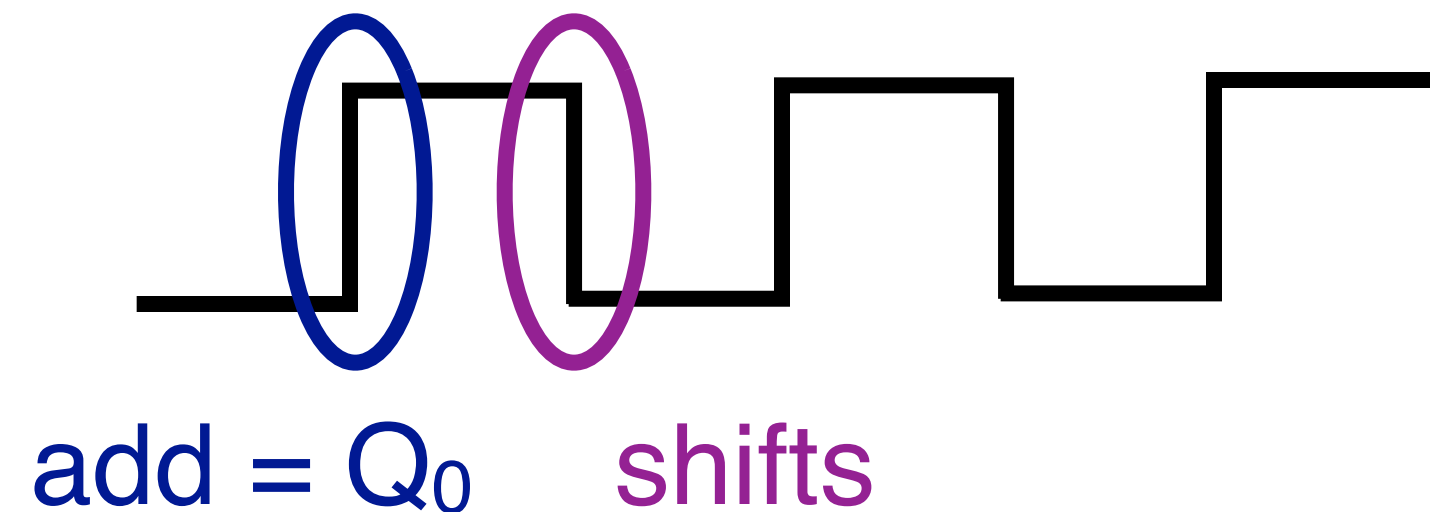
# Control Logic and Counter


- Finite state machine, designed as we have done in class
- Separate into counter (which we can design) and control logic
  - Counter: set to  $n$ , decrement to 0 (NOR = done)
  - Control logic: if  $Q_0 = 1$ , add and load new value
    - ▶ route  $Q_0$  to add and load signals
    - ▶ Shifts - always shift.



# Binary multiply: a better circuit?

- We're only really adding  $n$  bits at a time
  - Can we get away with an  $n$  bit adder?
- As the number of bits in  $P$  increases, the number of bits in  $Q$  decreases
  - Perhaps we can utilize this as well.
- Consider the following hardware:

# Binary multiply: a better circuit?

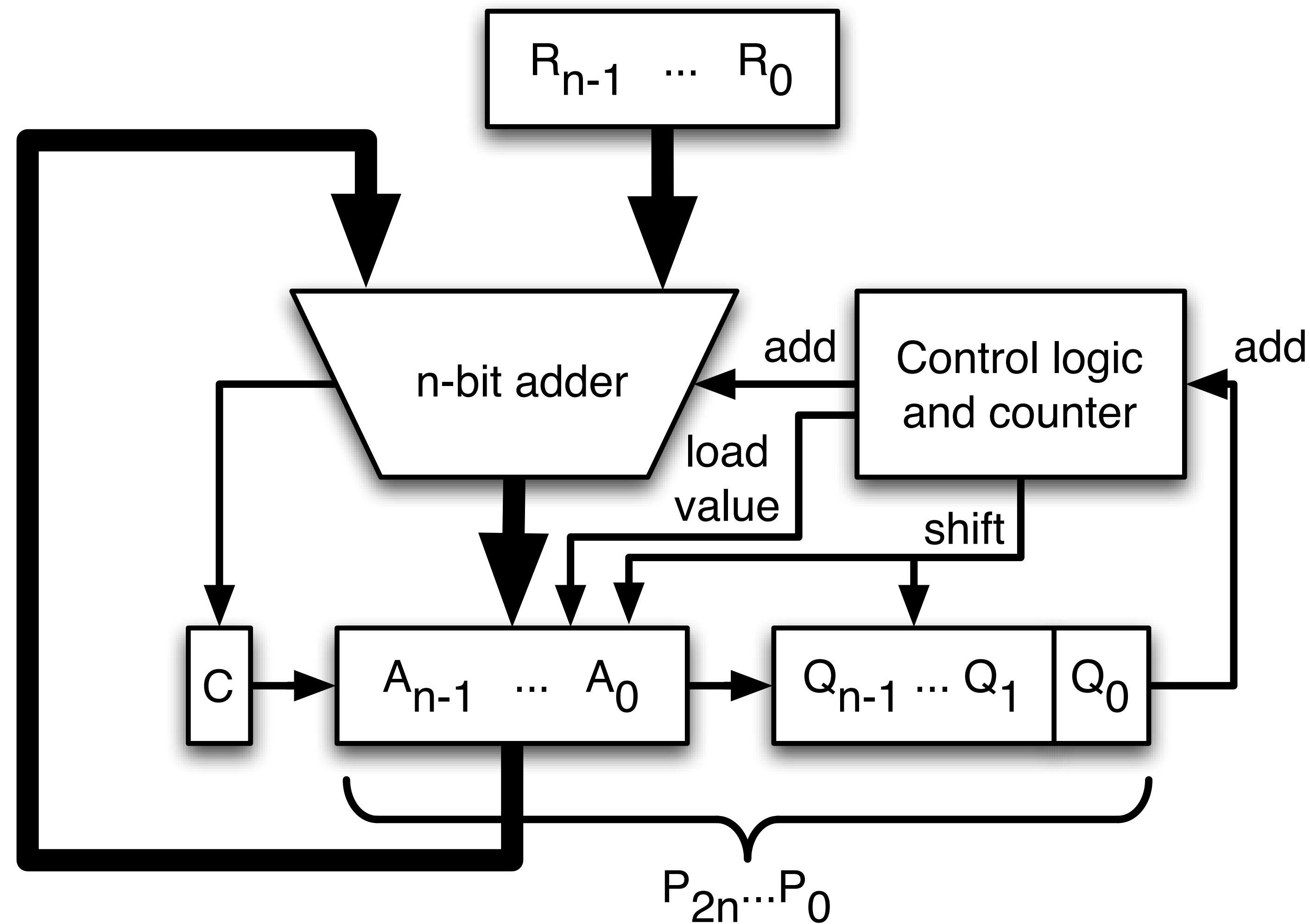

# Binary multiply: a better circuit?

- All registers, and the adder, are now  $n$  bit
- New register A holds partial product.
- Carry bit is shifted into MSB of A
- LSB of A is shifted into MSB of Q
- A and Q together make partial products P

# Signed Multiplication

- Check sign of R and Q
- Make positive, if necessary
- Perform multiplication as before
- Change sign of result P if necessary
  - i.e. if  $R_{n-1} \oplus Q_{n-1} = 1$ , result should be negative.
- Easier way: Booth algorithm
  - Takes advantage of some cool math



# The booth algorithm

- Consider a number containing a string of 1s
  - eg. 011110
- Recall (from 2's complement work):
$$1111 = 10000 - 1$$
- It is also true that
$$011110 = 100000 - 10$$
$$2^4 + 2^3 + 2^2 + 2^1 = 16 + 8 + 4 + 2 = 30$$
$$= 32 - 2$$
$$= 2^5 - 2^1$$

# The booth algorithm

When the multiplier has a string of 1s,  
add at the multiplicand at the start of the string  
subtract the multiplicand at the end of the string


Identifying the ends of a string of 1s

Starts with "01", ends with "10"


This also allows us to multiply signed numbers  
because we are subtracting.

e.g.:  $100001 = -100000 + 10$

# The booth algorithm

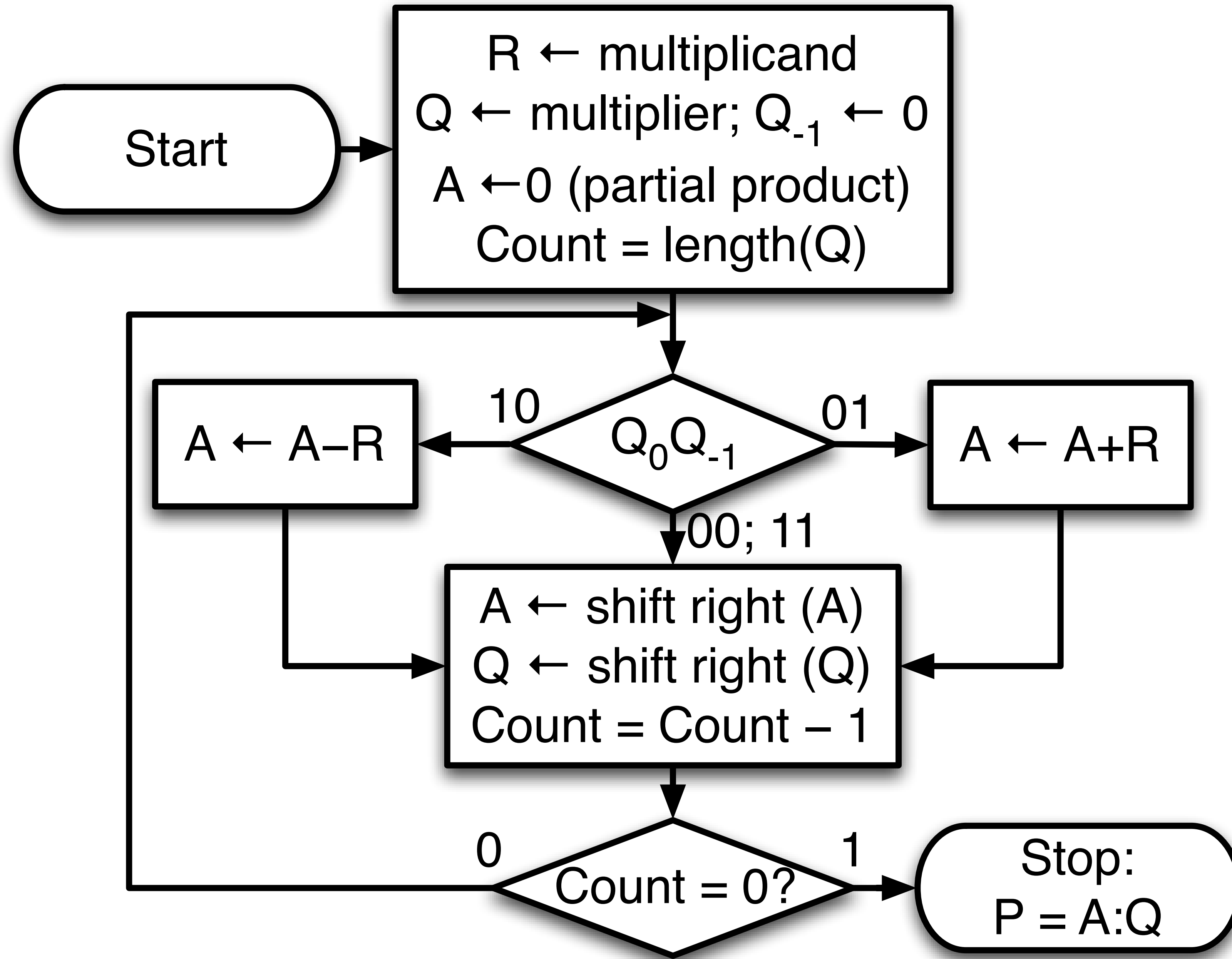

# The booth algorithm implementation

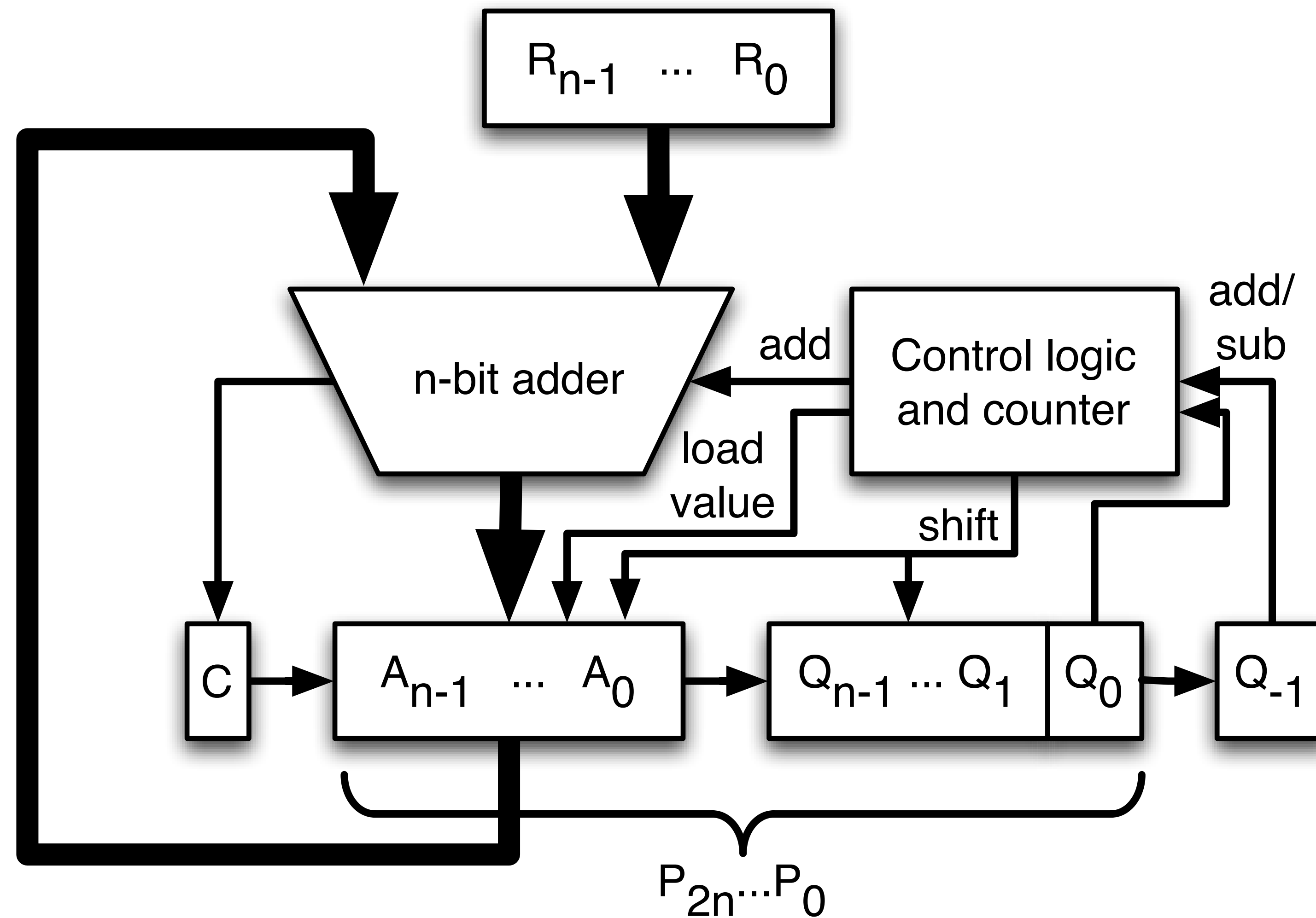

# But wait...


- This algorithm needs to handle positive AND negative numbers, but
- Shift right could turn negative into positive!

1100  $\rightarrow$  shift right  $\rightarrow$  0110;      -4  $\rightarrow$  6

- We want to retain the sign when we shift
- *Arithmetic* shift right: replicate the sign bit.

1100  $\rightarrow$  arithmetic shift right  $\rightarrow$  1110;      -4  $\rightarrow$  -2

# Shifts

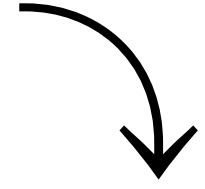- Logical shift: Shift in a "0" from either direction
- Arithmetic shift: maintain sign bit
  - Shifting right: replicate the sign bit, drop the LSB
    - ▶  $\hookrightarrow Q_n \rightarrow Q_{n-1} \rightarrow \dots \rightarrow Q_1 \rightarrow Q_0$  
    - ▶ becomes  $Q_n \ Q_n \ Q_{n-1} \ \dots \ Q_1$
  - Shifting left: Retain the sign bit, shift in a "0" from the right.
    - ▶  $\hookrightarrow Q_n \ Q_{n-1} \leftarrow Q_{n-2} \ \dots \ \leftarrow Q_0 \leftarrow 0$
    - ▶ becomes  $Q_n \ Q_{n-2} \ \dots \ Q_1 \ 0$

# The booth algorithm : Example

$$10111 \times 10011, (-9) \times (-13) = +117 = 01110101$$

C	A	Q	Q-1	Next Function
5	00000	10011	0	Subtract
	01001	10011	0	Arith. shift
4	00100	11001	1	Arith. shift
3	00010	01100	1	Add
	11001	01100	0	Arith. shift
2	11100	10110	0	Arith. shift
1	11110	01011	0	Subtract
	00111	01011	0	Arith. shift
0	00011	10101	1	Done



# Unsigned division

# Again, go back to grade 3:

$$147 \div 11 = 13, \text{ remainder } 4$$

# Divisor

$$\begin{array}{r} 00001101 \\ 1011 \overline{) 10010011} \end{array}$$

# Quotient

# Dividend


# Partial Remainders

# Remainder

# Division

- multiplication is repeated addition of the multiplicand based on whether or not the multiplier is 0 or 1
- division is repeated subtraction of the divisor from the dividend
  - If the result is negative you took away too much and the quotient should be 0 at that bit position
  - add back the divisor
  - If the result is positive, you didn't subtract too much so the quotient should be 1 at that bit position

# Procedure: Unsigned division

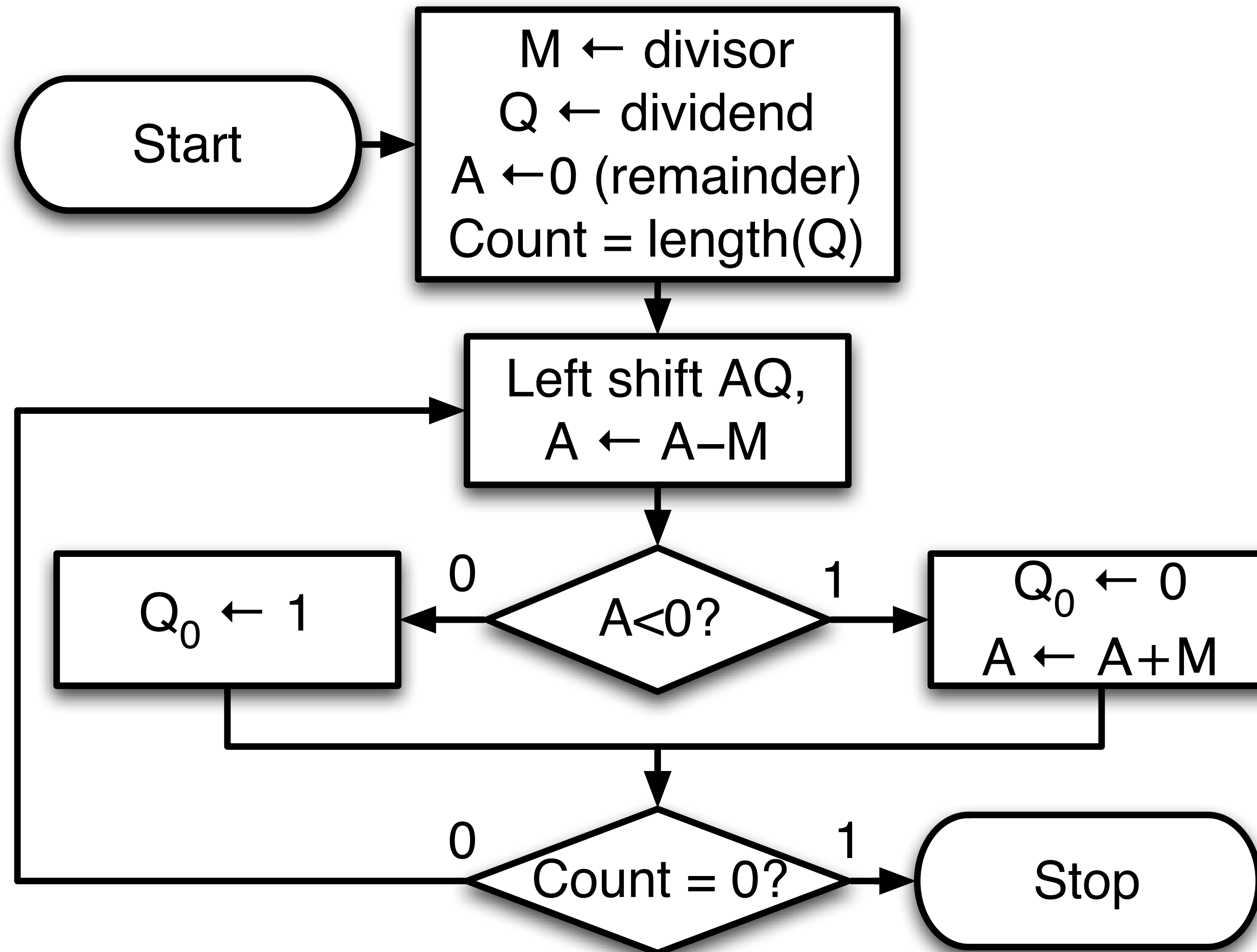

# Things to consider

- This algorithm assumes  $M > Q$
- A is  $n+1$  bits long
- Shifting A and Q together
  - same idea as in multiply
- Successive subtraction
  - Each time, if the result is negative, subtracted too much so add back again.
- Use a counter, start at "n"
- "Done" when counter reaches 0
  - Quotient is in "Q", Remainder is in "A"

# Example: $1000/11=10r10$ ( $8/3=2r2$ )

C	A	Q	Function
4	00000	1000	Start
	00001 ←	000□	shift AQ
	11110	000□	$A \leftarrow A - M$
3	00001	0000	$Q_0 \leftarrow 0, A \leftarrow A + M$
	00010 ←	000□	shift AQ
	11111	000□	$A \leftarrow A - M$
2	00010	0000	$Q_0 \leftarrow 0, A \leftarrow A + M$
	00100 ←	000□	shift AQ
	00001	000□	$A \leftarrow A - M$
1	00001	0001	$Q_0 \leftarrow 1$
	00010 ←	001□	shift AQ
	11111	001□	$A \leftarrow A - M$
0	00010	0010	$Q_0 \leftarrow 0, A \leftarrow A + M$


$$00001 - 11 = 11110$$

$$00010 - 11 = 11111$$

$$00100 - 11 = 00001$$

$$00010 - 11 = 11111$$

# Hardware for division

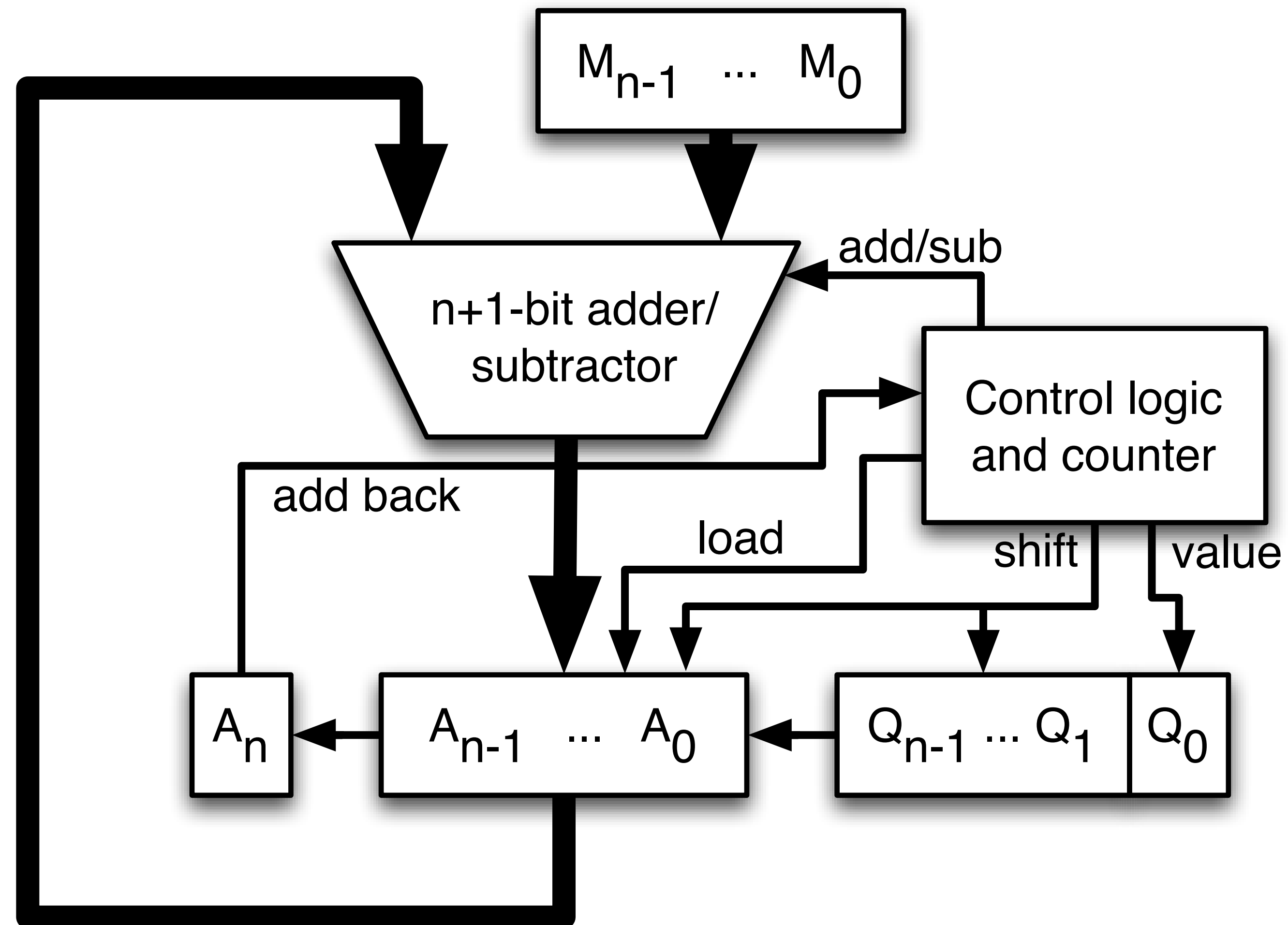

# Floating Point Numbers

- So far we've dealt with integers
- Need to allow computers to handle decimals, big numbers and small numbers
- We'll cover this later in the course, somewhat abstractly



# Where are we now?

- We've built all the parts we need to start assembling them into a computer
  - Registers
  - Memory (sort of - we'll do more)
  - ALU and other math bits
- We need to do some work before we start assembling
  - What will this computer do, and how?
  - How to move data around in the computer?
- Next: Assembly Language.